

# 总复习

2023年12月29日 11:03

## 导论

Moore's law: The observation that the number of **transistors** in a dense IC **doubles** approximately **every two years**

### Characteristics of AIC:

- operational amplifiers, voltage and current circuits
- OPAMP determines the whole performance of IC(**core** circuits)

### Challenge in AIC:

- sensitive to noise, crosstalk and other interferences
- heavy second order effects

### Challenge in DIC:

- multiple levels of abstractions
- multiple and conflicting constraints: low cost and high performance
- short design time

ISSCC: IEEE international Solid-State Circuits Conference

## 工艺流程

### operations:

- **Wafer**: 产生合适类型的衬底
- **Photolithography (光刻)**: 精确地划分各个区
- **Oxidation, deposition, ion implantation (氧化、沉积、离子注入)**: 给晶圆添加材料
- **Etching (蚀刻)**: 去除材料

## | CMOS Fabrication Steps

### N-well Silicon-gate CMOS


- P衬底上形成N-well
- 确定有源区(active)、场区(field), 场区隔离(isolation)
- 制备MOS管: 阈值电压调节, 自对准结构、LDD

- 元件互连
- 钝化


Self-aligned:

PMOS: n-well -> gate oxide and polysilicon -> source/drain junctions

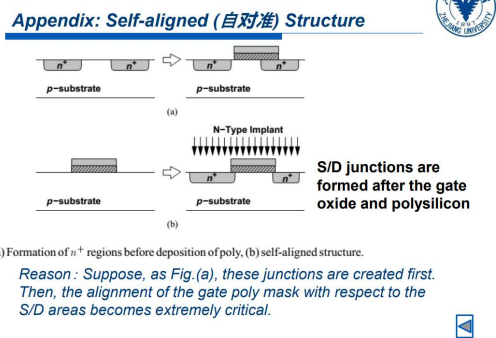
- Make S/D regions implanted at precisely the edges of gate area



layout of a PMOS电流源负载差分对

 

layout的串并联

 

器件模型

| Diode


$$I_D = I_S(\exp(V_D/\phi_T) - 1)$$

jo

耗尽层电容:  $C_j = \frac{C_{j0}}{(1-V_D/\phi_0)^m}$

Breakdown:  $BV \approx \frac{\epsilon_{Si}(N_A+N_D)}{2qN_A N_D} E_{max}^2 E_{max} = 3 \times 10^5 V/cm$


## MOS

 

深线性区: 作电阻,  $R_{on} = \frac{1}{\mu_n C_{OX} W/L (V_{GS} - V_{TH})}$


饱和区: 作电流源,  $I_D = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$

PMOS的电流驱动能力更差,  $\mu_p < \mu_n$

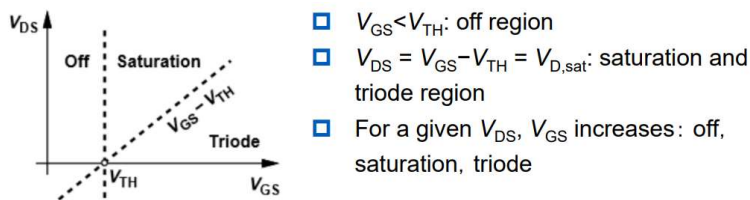

## 跨导

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \big|_{V_{DS}=const} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{1}{R_{on}}$$

 

## Body effect

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|})$$

参量  $\gamma$  与衬底浓度有关,  $N \uparrow \Rightarrow \gamma \uparrow$

$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} = \eta g_m$$


## 沟道调制效应

记得跨导也要  $\times (1 + \lambda V_{DS})$

$$r_{ds} = \frac{1}{I_{DS} \lambda}$$

$L \uparrow \Rightarrow \lambda \uparrow$

 Early Voltage:  $V_E L = \frac{I_{ds}}{g_{ds}} = \frac{1}{\lambda}$




Slope is 1/4!

## 弱反型

当  $V_{GS} < V_{TH}$ , MOSFET 不会马上关断,  $I_D = I_0 \exp\left(\frac{V_{GS}}{\zeta V_T}\right)$ ,  $g_m = \frac{I_D}{\xi kT/q}$
 
## 高频电容

耗尽层 (源/漏与体):  $C_j \times Area + C_{jsw} \times Perimeter$



栅-沟道电容:  $C_1 = W_{eff} L_{eff} C_{ox}$

栅-源/漏交叠电容:  $C_3/C_4 = CGXO \cdot W_{eff} = C_{ov} W$  ( $C_{ov} = LC_{ox}$ )

按区域:

- 关断区:  $C_{GS} = C_3$ ,  $C_{GD} = C_4$ ,  $C_{GB} = C_1 // C_2$
- 三极管区:  $C_{GS} = C_3 + 1/2 C_1$ ,  $C_{GD} = C_4 + 1/2 C_1$ ,  $C_{GB}$  不考虑
- 饱和区:  $C_{GS} = C_3 + 2/3 C_1$ ,  $C_{GD} = C_4$ ,  $C_{GB}$  不考虑

## PMOS vs. NMOS

在CMOS工艺中, PMOS劣(inferior)于NMOS:

- Lower mobility of holes
- Lower output resistance


# 模拟基本单元

## Switch

dummy管:

- 减少clock feedthrough
- 减轻沟道充电效应

CMOS Switch:

 


- feedthrough被抵消了
- 更大的动态范围
- 更小的 $r_{ON}$
- 要求互补时钟
- 更大面积
 
## 二极管

$$r_o = \frac{1}{g_m + g_{mb} + g_{ds}}$$


当 $I_D$ 固定（接恒流源时），令 $V_{ON} = \sqrt{2I_D/\beta}$ ，则 $V_{DS} = V_{GS} = V_{ON} + V_{TH}$



$$V_{bias} = 2V_{ON} + 2V_{TH}$$
 
## 电流源


Cascode电流源：看 $r_{out}$ 时，M1管子相当于一个漏源电阻， $r_o = (g_{m2} + g_{mb2})r_{ds2}r_{ds1}$



多级Cascode：把最底下的当作电阻，上面有多少级就 $\times$ 多少个 $g_m r_o$

在电流源当中 $V_{ON}$ 作为一种设计参数，已知。

1.

 

2. 上图M4和M2的源端对称，因此M1工作电压在 $V_{ON} + V_T$ ，降低M1管的 $V_{DS}$ ：




## Mismatch问题


- 沟道效应调制:  $V_{DS2}$  取决于负载电路-----增大L、Cascode电流镜
- M1、M2失配
- 版图影响

## Cascode电流镜

1. 见ch. 电流源（工作电压太高，但是M3的Vb不用自己设计）

 


2. Low-voltage Cascode

 


$$V_b \geq V_{OD1} + V_{OD0} + V_{TH0}$$

Generation of vb:

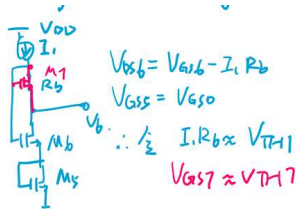

3. 现行Cascode电流镜

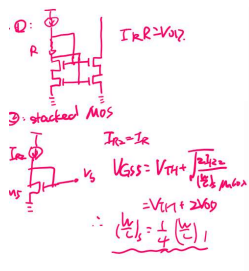


## Voltage biasing

Temperature variation:  $TC(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$

Supply Rejection:  $S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}}$

电阻-MOS 分压器

 

## MOS-only 分压器

$$I_{D1} = I_{D2}$$


$$\frac{\beta_1}{2} (V_{ref} - V_{SS} - V_{THN})^2 = \frac{\beta_2}{2} (V_{DD} - V_{ref} - V_{THP})^2$$

the reference voltage:

$$V_{ref} = \frac{V_{DD} - V_{THP} + \sqrt{\beta_1 / \beta_2} (V_{SS} + V_{THN})}{\sqrt{\beta_1 / \beta_2} + 1}$$

or knowing the reference voltage and the power supply voltages gives
 
$$\frac{\beta_1}{\beta_2} = \left[ \frac{V_{DD} - V_{ref} - V_{THP}}{V_{ref} - V_{SS} - V_{THN}} \right]^2$$




$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{DD} - V_{THP} + \sqrt{\beta_1 / \beta_2} (V_{SS} + V_{THN})}$$

$$TC(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\beta_1 / \beta_2} + 1} \cdot \left[ -\frac{\partial V_{THP}}{\partial T} + \sqrt{\beta_1 / \beta_2} \frac{\partial V_{THN}}{\partial T} \right]$$

## Bias Current Generation

### Self-biasing

 

$$I_{out} = KI_{REF}$$


## Temperature Independent Reference

### Negative-TC Voltage

bjt

### Positive-TC Voltage

差分对

 

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_t \ln \frac{nI_0}{I_{S1}} - V_t \ln \frac{I_0}{I_{S2}}$$

$$= V_t \ln n$$

$$\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

是PTAT常用电路。




$$\Delta V_{BE} = V_{BE1} - V_{BE2} = V_T \ln \left( \frac{I_1}{I_2} \right) - V_T \ln \left( \frac{I_2}{I_2} \right)$$

$$\frac{A_{E2}}{A_{E1}} = n \quad \frac{I_{S2}}{I_{S1}} = n$$


$$V_R = \Delta V_{BE} = V_T \ln \left( \frac{I_1}{I_2} \cdot \frac{I_{S2}}{I_2} \right)$$

$$= V_T \ln \left( \frac{I_{S2}}{I_{S1}} \right) = V_T \ln \left( \frac{A_{E2}}{A_{E1}} \right) = V_T \ln n$$
 
$$I_O = I_2 = \frac{\Delta V_{BE}}{R} = \frac{V_T}{R} \ln n$$



## 带隙基准 (BGR)

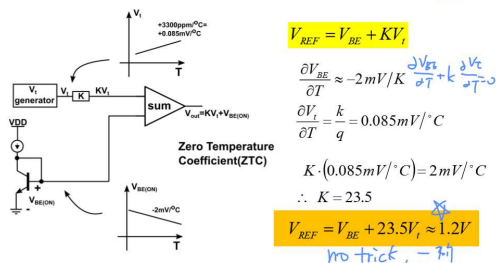

## 单级运放

放大器  $R_{in} \rightarrow \infty$ ,  $R_{out} \rightarrow 0$

## Common-Source

### 电阻负载

$$A_v = -g_m R_D = -\mu_n C_{ox} W/L (V_{in} - V_{TH}) R_D (// r_o)$$

$$R_{out} = (r_o // R_D); R_{in} = \infty$$


Intrinsic Gain:  $R_D \rightarrow \infty, A_v = -g_m r_o$

### 二极管负载

$$\text{二极管的等效电阻 } R_D = \frac{1}{g_m} // \frac{1}{g_{mb}} // r_o$$


其他的就跟电阻负载一样分析就好。

Output Swing: 二极管负载会牺牲一部分电压，swing减小。

 

注意，N管有体效应，P管一般没有。

Enhancement: 电流源 $I_S$ 可以用PMOS实现。

 


## 电流源负载

电流源的等效电阻是 $r_o$ ，栅接交流地。

如果是理想电流源， $A_v = -g_m r_o = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \cdot \frac{1}{\lambda I_D} \propto \frac{1}{\sqrt{I_D}}$ ，小电流大增益（代价是低速高noise）

## Push-Pull 反相器

 


$$A_v = -(g_{m1} + g_{m2})(r_{o1} // r_{o2})$$

## Source Degeneration

接一个源级负反馈电阻 $R_S$ ， $G_m = -\frac{g_m}{1 + g_m R_S}$

$$R_{out} = r_o + R_S + (g_m + g_{mb})R_S r_o \approx (g_m + g_{mb})R_S r_o$$


相当于本征增益乘 $R_S$ （阻抗倍增小效应）（Cascode）

 

## Source-Follower


高输入阻抗、低输出阻抗，增益小于等于1

用于降低CS的高输出阻抗。

 

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb})R_S}$$

## 电流源负载

 


只能用N管。

$$A_v = \frac{g_m}{g_m + g_{mb}}$$

$$R_{out} = \frac{1}{g_m + g_{mb}}, \text{ 联想电流源负载的CS.}$$

## Common-Gate

低输入阻抗，高输出阻抗

 

## Cascode Stage

**Cascode Stage**

- CS stage + CG stage
- $M_1$ : the input device  $V_{in} \rightarrow I_1 = g_{m1} V_{in}$
- $M_2$ : the cascode device, routing the current to  $R_D$   $I_1 = I_2$
- $V_{out} = V_{DD} - I_2 R_D$
- **telescopic cascode**

$M_1, M_2$ : in saturation  $\lambda = \gamma = 0$

- $V_{in}: \Delta V \rightarrow I_{D1}: g_{m1} \Delta V$
- $V_X$  falls  $g_{m1} \Delta V (1/g_{m2})$
- $V_{out}: g_{m1} \Delta V R_D$  as in a simple CS stage

62

如果是M2输入，相当于接无穷大的源级负反馈， $V_{out}=0$ 。

# 差分放大器

## 差分的好处

- 提高swing
- 减少信号间耦合

- 减少coupled noise
- Rejection of supply noise
- 容易偏置
- 更高的线性度
- 更大的面积

## 输入范围

$$\text{ICMR: } V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH3}, V_{DD}]$$

Lower limit: M3 saturation region; Upper limit: M1\M2 triode region


## Output swing

$$[\max(V_{in,CM} - V_{TH}, V_{DD} - I_{SS}R_D), V_{DD}]$$

## Half-Circuit

$$V_X - V_Y = -g_m(R_D // r_o)(V_{in1} - V_{in2}), \text{ 无所谓是否完全差分}$$


两种改进:

 

## 共模响应


差分对并不是完全对称、微电流具有有限的输出阻抗。

### 1. Output Impedance $R_{SS}$

 

$$A_{v,CM} = -\frac{R_D/2}{R_{SS} + 1/(2g_m)}, \text{ 并联的管子 } G_m = 2g_m$$

### 2. $g_{m1} \neq g_{m2}$
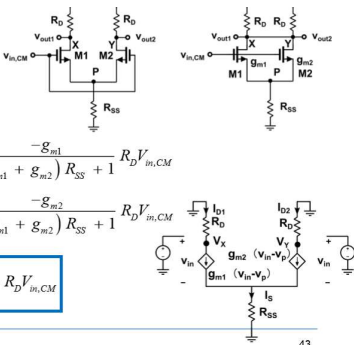
$$\begin{aligned}
 (g_{m1} + g_{m2})(V_{in,CM} - V_P) &= I_{D1} + I_{D2} \\
 (g_{m1} + g_{m2})(V_{in,CM} - V_P)R_{SS} &= V_P \\
 \Rightarrow V_P &= \frac{(g_{m1} + g_{m2})R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}} V_{in,CM} \\
 \Rightarrow V_X &= -g_{m1}(V_{in,CM} - V_P)R_D = \frac{-g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM} \\
 V_Y &= -g_{m2}(V_{in,CM} - V_P)R_D = \frac{-g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM} \\
 \Rightarrow V_X - V_Y &= -\frac{g_{m1} - g_{m2}}{1 + (g_{m1} + g_{m2})R_{SS}} R_D V_{in,CM}
 \end{aligned}$$


$$A_{CM-DM} = \frac{\Delta g_m R_D}{1 + 2g_m R_{SS}} \quad (g_m = \frac{g_{m1} + g_{m2}}{2})$$

$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_m}{|\Delta g_m|} (1 + 2g_m R_{SS})$$


### 3. 二极管负载的差分对

$$A_v = -g_{m1}(g_{m3} // r_{o3} // r_{o1})$$

### 4. Cascode负载的差分对

$$A_v = g_{m1}[(g_{m3} // r_{o3} // r_{o1}) // (g_{m5} // r_{o5} // r_{o7})]$$

### 5. OTA

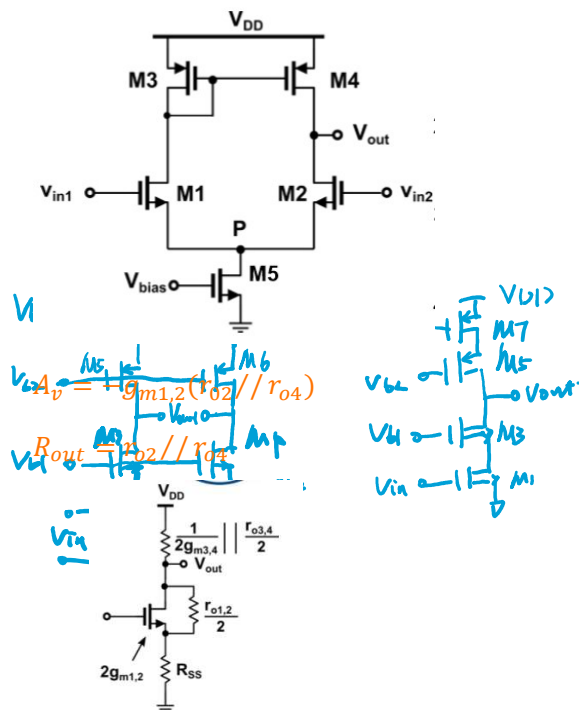

$$A_{CM} = \frac{1}{R_{SS} + 1/(2g_{m1,2})} (1/(2g_{m3,4}) // (r_{o3,4}/2) // (r_{o1,2}/2))$$

$$CMRR = (1 + 2g_{m1,2}R_{SS})g_{m3,4}(r_{o1,2} // r_{o3,4})$$


# OPAMP

## Ideal op-amp

- 压控电压源
- 增益无穷大
- 无限输入阻抗
- 零输出阻抗

## 一阶运放

### Basic Topologies

 


- Low-frequency gain:  $A_O = g_{mN} r_{out} = g_{mN} (r_{ON} // r_{OP}) < g_{mN} r_O$
- Bandwidth:  $\omega_1 = \frac{1}{C_L R_{out}} = \frac{1}{(r_{O2} // r_{O4}) C_L}$   $\omega_u = \frac{g_{mN}}{C_L}$
- Output Swing (single-side):  $V_{DD} - 3V_{OV}$
- Mirror pole in single ended

## 二阶运放

Stage1: High Gain

Stage2: High Swing

 

$$A_V = A_{V1} \times A_{V2}$$


$$A_V = g_{m1,2} (r_{O1,2} // r_{O3,4}) g_{m5,6} (r_{O5,6} // r_{O7,8}) \quad A_V = g_{m1} (g_{m3} r_{O3} r_{O1} // g_{m5} r_{O5} r_{O7}) g_{m9} (r_{O9} // r_{O11})$$

$$V_{out,min} = V_{ds7,sat}$$

$$V_{out,max} = V_{DD} - V_{ds5,sat}$$

$$V_{out,min} = V_{ds11,sat}$$

$$V_{out,max} = V_{DD} - V_{ds9,sat}$$

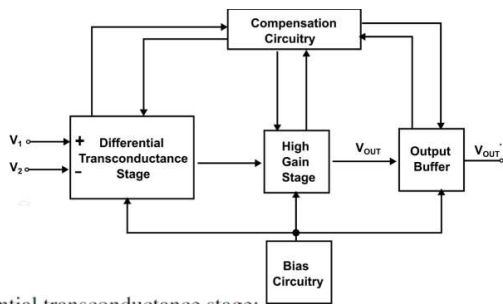

ferential transconductance stage:

差分跨导级：输入，有时提供差分到单端的转换；


高增益级：由opamp和输入级提供电压增益

输出缓冲：如果opamp需要驱动低阻抗

compensation电路：保持OP稳定，当阻性负反馈。
 
## 稳定性考量


- Feedback systems suffer from potential instability and they may oscillate!!!



- Closed-loop transfer function:  $\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$
- When  $\beta H(s) = -1$ , the closed-loop "gain" goes to infinity  $\rightarrow$  oscillate
- Barkhausen's Criteria:  $|\beta H(j\omega)| = 1$   
 $\angle \beta H(j\omega) = -180^\circ$
- Negative feedback itself provides 180 phase shift
- Loop transmission determines the stability issue

## Miller 补偿


### -- Miller Compensation

 

Stage 1: High output impedance  
Stage 2: A moderate gain

dominating pole: 节点E的大电容

中电容导致低频极点-移除输出极点

 

## 其他问题


### Input Range limitations

### slew rate

## 反相器

## 基本结构

推挽式结构

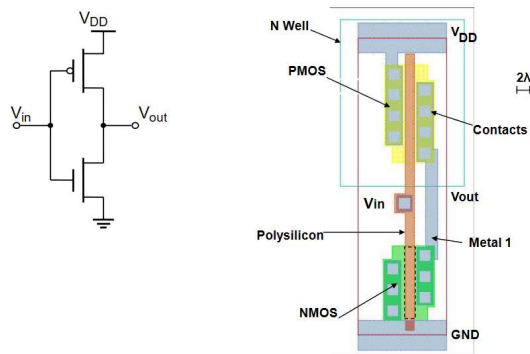


漏端相连，最小尺寸 $2\lambda$

PN管的宽长比是不一样的，P更宽


## 一阶直流分析

采用开关模型。（N管高于阈值电压导通，懂得都懂）

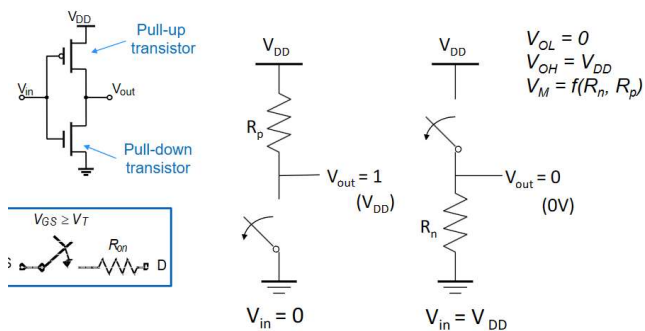


- 摆幅是rail to rail ( $V_{DD}$ -GND) 高噪声容限
- ratioless 无比电路
- 静态功耗小（ $V_{DD}$ 和GND之间没有直接通路）噪声和干扰不敏感
- 低输出阻抗
- 输入阻抗大

## VTC(Voltage Transfer Characteristics)

 



## 动态特性（速度）

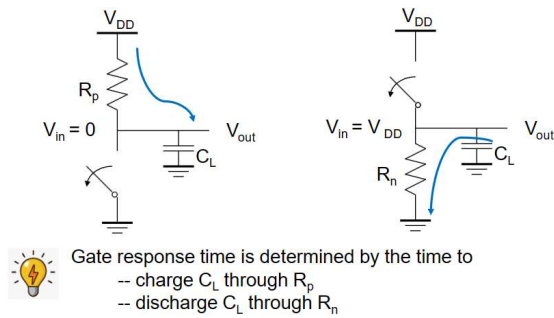

减小输出电容或者减小  $R_{on}$  (增大W/L)

瞬态响应主要由输出电容决定。

## 静态特性

### 开关阈值 ( $V_M$ )


假设  $V_{in} = V_{out}$ ，两个管子都在饱和区。

$V_M \approx r V_{DD} / (1 + r)$ ,  $r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$  电子和空穴的饱和速度； $r$ 是相对驱动强度，基本上完全取决于宽度比。

为了让  $r$  接近1，P的宽度会做的比N大。

### 噪声容限


把斜率为-1的点当作截止点。

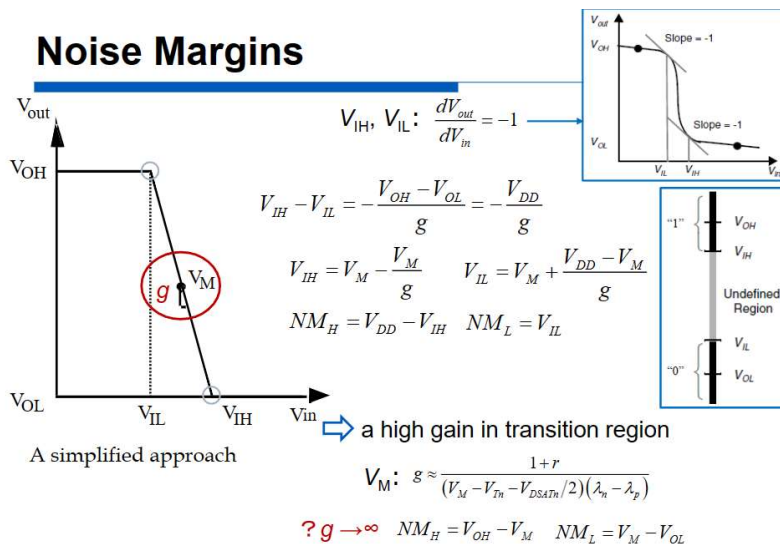

工程上是拿M点斜率作交点得到IH和IL。

$$V_M: g \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

### 工艺的影响

 


## 电源电压的影响

降低VDD改善增益，但  $V_{DD} > (2\alpha_0)kT/q$
 
## Dynamic Behavior

以CMOS为例，C<sub>inc</sub>是第一级反相器的电容，包括栅漏电容和漏底电容；C<sub>ext</sub>是导线电容和二级反相器的电容，包括两个栅源电容。



## 一阶传播延时

- Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance

$$t_p = \int_{v_1}^{v_2} \frac{C_L(v)}{i(v)} dv = f(R_n, C_L)$$

**first-order linear RC-network:**

$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L$$

$$t_{pLH} = \ln(2) R_{eqp} C_L = 0.69 R_{eqp} C_L$$

$$t_p = (t_{pHL} + t_{pLH}) / 2 = 0.69 C_L (R_{eqn} + R_{eqp}) / 2$$


$\Rightarrow t_{pHL} = t_{pLH} \quad R_{eqn} = R_{eqp}$

**a symmetrical VTC**

输出高到低看n，低到高看p

$$t_{pHL} \approx 0.52 \frac{C_L}{(W/L)k_n V}$$
 
## ? How to manipulate or optimize the delay?




Trade-off between delay and consumption

为了减小传播延时:

1. 降低CL, keep the drain diffusion as small as possible
2. 增加宽长比
3. 增大VDD
 
## NMOS/PMOS Ratio

- Symmetrical VTC and  $t_{pHL} = t_{pLH}$ :  $\beta = (W/L_p)/(W/L_n) = 3 \sim 3.5$
- If speed is the only concern, **reduce** the width of the PMOS device



$t_p = (t_{pHL} + t_{pLH})/2$   
widening PMOS degrades  $t_{pHL}$  due to larger parasitic capacitance

$$\frac{\partial t_p}{\partial \beta} = 0 \Rightarrow \beta_{opt} = \sqrt{r \left( 1 + \frac{C_w}{C_{dn1} + C_{gn2}} \right)}$$

$$C_w \Rightarrow \beta_{opt} = \sqrt{r}$$

- $\beta$  of 2.4 ( $= 31 \text{ k}\Omega / 13 \text{ k}\Omega$ ): symmetrical response
- $\beta$  of 1.6 to 1.9: optimal performance

实际上最佳点的偏移: 宽长比改变后不仅电阻改变, 寄生电容也改变了。

- Divide capacitive load,  $C_L$ , into  $C_L = C_{int} + C_{ext}$ 
  - $C_{int}$ : intrinsic (self-loading) cap - diffusion and gate-drain (Miller) effect
  - $C_{ext}$ : extrinsic load cap- wiring and fan out
- $t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$
- **intrinsic delay** (unloaded,  $C_{ext}=0$ )  
 $t_{p0} = 0.69 R_{eq} C_{int}$



## □ Size factor: S (reference gate)

$$C_{int} = SC_{iref} \quad R_{eq} = C_{eq}/S$$

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int})$$

$$= 0.69 R_{ref} C_{iref} (1 + C_{ext}/C_{int})$$

$$= t_{p0} (1 + C_{ext}/SC_{iref})$$

--  $t_{p0}$ : the size of gate **X**  
technology and layout **✓**

--  $S \uparrow, t_p \rightarrow t_{p0}$

## 反相器链

The delay of the  $j$ -th inverter stage:


$$t_{p,j} = t_{p0} (1 + C_{g,j+1}/(\gamma C_{g,j})) = t_{p0} (1 + f_j/\gamma)$$

and  $t_p = t_{p1} + t_{p2} + \dots + t_{pN} \Rightarrow t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1}/(\gamma C_{g,j}))$

$$\frac{\partial t_p}{\partial C_{g,j}} = 0 \Rightarrow C_{g,j+1}/C_{g,j} = C_{g,j}/C_{g,j-1} \quad C_{g,j} = \sqrt[N]{C_{g,j-1} C_{g,j+1}}$$



 □ The optimum size of each inverter is the geometric mean of its neighbors sizes.



□ The optimum size of each inverter will have the same effective fan-out and the same delay


$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$

$F$ : the overall effective fan-out of the circuit ( $F = C_L/C_{g,1}$ )

□ The minimum delay through the inverter chain is

$$t_p = N t_{p0} (1 + \sqrt[N]{F}/\gamma)$$

### Example

 

$C_L/C_1$  has to be evenly distributed across  $N = 3$  stages:  $f = \sqrt[3]{8} = 2$

## 最佳阶数N

□ What is the optimal value for  $N$  given  $F (=f^N)$ ?

$$t_p = N t_{p0} (1 + \sqrt[N]{F}/\gamma)$$

- if  $N$  is too large, the intrinsic delay of the stages becomes dominate
- if  $N$  is too small, the effective fan-out of each stage becomes dominate

$$f = e^{1+\gamma/f}$$

- $\gamma=0$ : The optimal number of stages:  **$N=\ln(F)$**  ( $\gamma=0$ )  
the effective fanout of each stage  $f=2.71828=e$
- $\gamma=1$

# 导线

## Simplifications

- 忽略电感影响：导线电阻很大或者外加信号的上升下降时间很慢
- 导线间电容忽略，寄生电容模拟成接地电容：导线只在一段很短的距离靠在一起
- 当导线很短，截面很大或者互联材料的电阻率很低，可以采用只含电容的模型

现在的工艺通常使用Copper，但是Cu原子会扩散到硅并破坏FET；必须由diffusion barrier包围

## Lumped model 集总模型

要求比较短的导线

### RC trees

不包含回路！

共享路径电阻  $R_{ik} = \sum R_j, j \in [path(s \rightarrow i) \cap path(s \rightarrow k)]$

Elmore delay:  $\tau_{Di} = \sum C_k R_{ik}$

### 无分支RC树

$$\tau_{DN} = \sum C_i R_{ii} = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots R_i)$$

该模型可以用来近似一条电阻电容线，总长 $L$ ，被分割成 $N$ 段， $\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$ ,  $R = rL$ ,  $C = cL$

一条导线的延时是长度的二次函数。

分布式rc线的延时是集总模型的一半

# 组合逻辑门

## static CMOS

NMOS串联相当于AND，并联相当于OR，类似可推导出PMOS网络

根据DeMorgan定理，上拉网络和下拉网络对偶。


NAND2

- Delay is dependent on **the input patterns**
- Input: high to low transition
  - both inputs go low:  $0.69 R_p/2 C_L$
  - one input goes low:  $0.69 R_p C_L$
- Input: low to high transition
  - both inputs go high:  $0.69 2R_n C_L$

*Adding devices in series: slow down*  
*-> Wider device: avoid a performance penalty*

A gate with multi-in's: the combination of input that triggers **the worst-case conditions**

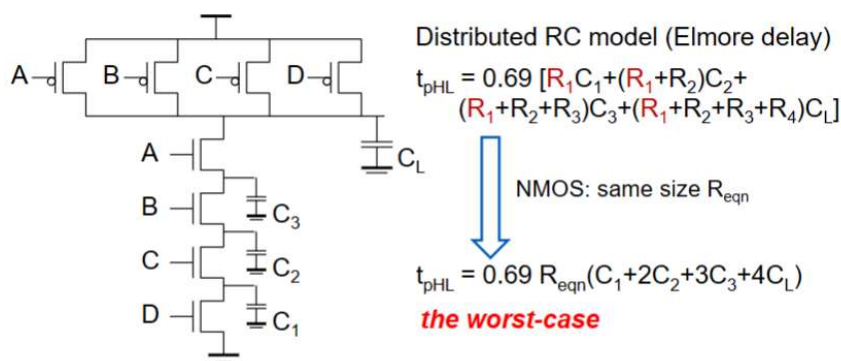对这一模型的简单分析表明，与噪声容限相类似，传播延时也取决于输入模式。例如考虑由低至高的翻转。可以看到有三种可能的输入情形可以使输出充电至  $V_{DD}$ 。如果两个输入都被驱动至低电平，那么两个PMOS器件都导通。这时的延时为  $0.69 \times (R_p/2) \times C_L$ ，因为这两个电阻并联。但这并不是最坏情形时由低至高的翻转，最坏情形发生在只有一个器件导通的时候，此时的延时为  $0.69 \times R_p \times C_L$ ，对于下拉路径，输出只有在 A 和 B 同时切换至高电平时才放电，因此就一阶近似而言延时为  $0.69 \times (2R_n) \times C_L$ 。换言之，增加串联的器件会使电路变慢，因而器件必须设计得较宽以避免性能下降。当确定一个多输入门的晶体管尺寸时，我们应当考虑能引起最坏情形的输入组合。



## Ratioed Logic

减少晶体管数，但降低稳定性，功耗升高。

仿NMOS门： $2N-N+1$ ，降低噪声容限，引起静态功耗

## Dynamic CMOS